

Application 6: External Multiplexed Display and Keypad Decoder

Purpose: To demonstrate and emulate the functions of a keypad and two digit LED display controller.

Goals:

1. Build and test a keypad and numeric LED display interface.
2. Load a program that will demonstrate the numeric LED display interface.
3. Modify the program and load additional code which will demonstrate the keypad decoder.

Component Description	Digi-Key part number
2) 2N3904 or 2N2222	2N3904-ND or 2N2222-ND
1) 741s240	DM74LS240N-ND
1) 4x4 matrix keypad	GH5004-ND
1) 2 digit LED display	P355-ND
9) 150 ohm 5% 1/4 watt resistor	
1) 1 Kohm 5% 1/4 watt resistor	


This application will be demonstrated in two phases: with the display only, and then with the keypad and display.

Display Controller Circuit Description

To drive an external 7 segment display using the trainer, the 8 output lines (numbered 0 to 7) would be the obvious choice. This would provide control for each of the 7 elements leaving one output line free. What if we want to drive two digits?. We need 7 more outputs which we don't have. The answer to this problem is to use a multiplexed scheme of driving the digits.

We can drive the anodes of each of the elements of the pair of 7 segment displays with the same outputs (one output per matching pair of segments) and use the 8th (bit 7) to select which display will turn on by driving the cathode of the desired digit to ground. This will allow us to display data on the left digit and turn the right one off, and vice-versa. If this is done rapidly enough it will appear as if both digits are showing simultaneously, due to "persistence of vision" in the human eye.

To lessen the load on the output port, the outputs drive a 74LS240 tri-state inverting buffer and the outputs of this go to the anodes of both digits of the display. The buffer's two enable lines are tied to the Primer's digital to analog (D/A) output and they tri-state the outputs when the D/A is output is 5V. This turns off the display which will be necessary when including the keypad in the circuit. When the D/A output is 0V the buffer is enabled

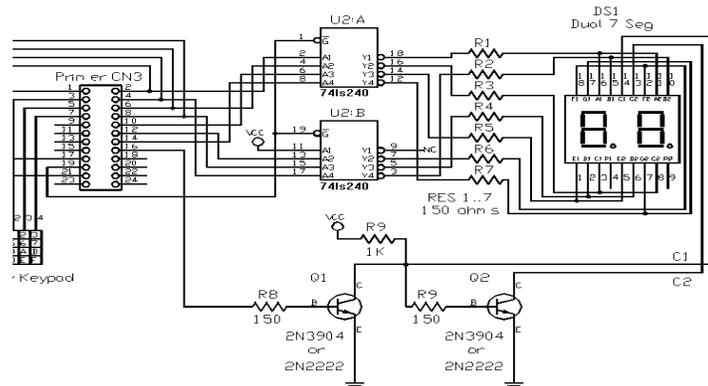

and the outputs go to the opposite logic level as their respective inputs.

If the buffer is enabled, bit 7 selects which display to turn on. If bit 7 is high, the voltage applied to the base of Q1 will bring the cathode for the left display to ground, causing it to turn on. When this happens, the base of Q2 is pulled to ground causing it to turn off, which turns off the display on the right. When bit 7 is low, this turns off Q1 which allows the base voltage of Q2 to rise and turn on the display on the right.

```
;
; External Multiplexed Display and Keypad Decoder program.
;
OPORT      EQU    11H      ;OUTPUT PORT
IPORT      EQU    12H      ;INPUT PORT
MOS        EQU    1000H    ;MOS CALL ADDRESS
DACSRV     EQU    0EH      ;D/A SERVICE

                ORG    0FF01H

LOOP:      IN      IPORT      ;READ DIP SWITCHES
            MOV     B,A
            CALL   HEXOUT     ;DISPLAY B
            JMP    LOOP

;
; Display the hex value of B on the LEDs. This routine must be
; called repeatedly in order for the data to be shown continuously,
; since it works on the principle of persistence of vision. The right
; digit is turned on and off first, then the left digit is turned on and off.
;
HEXOUT:    MOV     A,B        ;GET VALUE
            ANI    0FH        ;MASK OFF UPPER NIBBLE
            CALL   BIN7SG     ;CHANGE TO 7 SEG VALUE
            OUT    OPORT      ;SEND TO PORT
            CALL   FLSHDG     ;TURN ON DISPLAY MOMENTARILY

            MOV     A,B        ;GET ORIGINAL VALUE
            ANI    0F0H       ;NOW MASK OFF LOWER NIBBLE
            RRC
            RRC
            RRC
            RRC
            CALL   BIN7SG     ;CHANGE TO 7 SEG VALUE
            ORI    80H        ;SET BIT 7 SO LEFT DIGIT IS DISPLAYED
            OUT    OPORT      ;SEND TO PORT
            CALL   FLSHDG     ;TURN ON DISPLAY MOMENTARILY
            RET

;
; Change the binary number in A to its 7 seg. output pattern.
;
BIN7SG:    PUSH    H
            PUSH    D
            LXI    D,TAB7SG   ;POINT TO START OF TABLE
            MVI    H,0
            MOV    L,A        ;HL = OFFSET INTO TABLE
            DAD    D          ;ADD TABLE ADDR TO OFFSET
            MOV    A,M        ;GET OUTPUT PATTERN
            POP    D
            POP    H
            RET

;
; TRANSLATE TABLE FOR LED OUTPUT
;
TAB7SG:    DB      40H,79H,24H,30H
            DB      19H,12H,02H,78H
            DB      00H,18H,08H,03H
            DB      46H,21H,06H,0EH

;
; This flashes on and off the digit selected by bit 7 sent to OPORT.
```

```

;
FLSHDG:  PUSH    D
         PUSH    PSW
         CALL    LEDON      ;ENABLE LEDS
         LXI     D,0FFH
DELAY1:  DCX     D
         MOV     A,D
         ORA    E
         JNZ    DELAY1
         CALL    LEDOFF     ;DISABLE LEDS
         POP     PSW
         POP     D
         RET

;
; LEDON, LEDOFF, TURN ON/OFF THE LEDS THROUGH THE D/A OUTPUT
; 5V OUT TRI-STATES THE OUTPUTS OF THE 74LS240
; 0V OUT ENABLES THE OUTPUTS OF THE 74LS240
;
LEDON:   MVI     E,0        ;SEND OUT 0V
         JMP     LEDCTL
LEDOFF:  MVI     E,0FFH    ;SEND OUT 5V
LEDCTL:  MVI     C,DACSRV  ;D/A SERVICE
         CALL    MOS
         RET

```

Display Controller Software Description

The program will be described from the lowest level subroutine to the main routine.

LEDON, LEDOFF

The subroutine LEDON turns on the selected display by sending 0V from the D/A into the 74LS240 enables and LEDOFF turns them off by sending 5V.

FLSHDG

This CALLs LEDON, goes into a delay loop and then CALLs LEDOFF. This causes the display selected by bit 7 to display for the period of time of the delay.

BIN7SG

This converts the number in the accumulator (A), which is in the range of 0 to F hex, to its corresponding binary pattern which will be used by another routine to illuminate the desired display segments. Since each element of a digit is controlled by bits 0 to 6 the bit pattern sent to the output port will form specific patterns. The table TAB7SG used by this routine has these bit patterns for digits 0 to F.

HEXOUT

This displays the hex value of the B register on the displays. This routine must be called repeatedly in order for the data to appear to be shown continuously, since it works on the principle of persistence of vision. The upper 4 bits of B are masked off leaving only the lower 4 bits which are converted to the appropriate binary pattern using BIN7SG and and this pattern is sent to the output port. Since the patterns received from BIN7SG always have bit 7 cleared, this will turn on the digit on the right when FLSHDG is called. To display the left digit, the lower 4 bits are masked off of B and the upper 4 are moved to the lower 4 bit positions. This value is converted using BIN7SG, bit 7 of the result is set to 1, and it is sent to the output port. This time when FLSHDG is called, the left digit will be displayed since bit 7 is set.

The main loop of this first example gets its input from the DIP switches, copies the value to B, CALLs HEXOUT and loops back to read the DIP switches again.

Using the Program

Build the circuit and then check your work. Now load the following program into memory and run it. With all the DIP switches in the ON position the port will input 00 and this should be shown on the displays. The binary value input to the DIP switches will be shown in hex on the displays (refer to the section at the beginning of this manual which discusses binary to hex conversion). Set the DIP switches so one digit is different than the other.

It appears that both digits are showing at the same time. To show what is really happening, we can increase the delay in FLSHDG so we can see what is really happening. Change the byte at FF4B from 00 to FF and run the program again. The displays can now be seen alternating left to right with each change in bit 7. Note that the PRIMER's digital output LEDs reflect the data sent to the output port (output bits of 0 turn on these LEDs). Watch the binary pattern on bits 6 to 0 as the digits change.

Move the DIP switches to the off position so that "FF" is displayed (this guarantees that none of the inputs are being pulled low), stop the program and change the byte at FF4B back to 00 again.

ADDRESS	DATA	DESCRIPTION	FF2D	00		
FF01	D3	IN 12	FF2E	6F	MOV	L,A
FF02	12		FF2F	19	DAD	D
FF03	47	MOV B,A	FF30	7E	MOV	A,M
FF04	CD	CALL FF0A	FF31	D1	POP	D
FF05	0A		FF32	E1	POP	H
FF06	FF		FF33	C9	RET	
FF07	C3	JMP FF01				
FF08	01					
FF09	FF					
FF0A	78	MOV A,B				
FF0B	E6	ANI 0F				
FF0C	0F					
FF0D	CD	CALL FF27				
FF0E	27					
FF0F	FF					
FF10	D3	OUT 11				
FF11	11					
FF12	CD	CALL FF44				
FF13	44					
FF14	FF					
FF15	78	MOV A,B				
FF16	E6	ANI F0				
FF17	F0					
FF18	0F	RRC				
FF19	0F	RRC				
FF1A	0F	RRC				
FF1B	0F	RRC				
FF1C	CD	CALL FF27				
FF1D	27					
FF1E	FF					
FF1F	F6	ORI 80				
FF20	80					
FF21	D3	OUT 11				
FF22	11					
FF23	CD	CALL FF44				
FF24	44					
FF25	FF					
FF26	C9	RET				
FF27	E5	PUSH H				
FF28	D5	PUSH D				
FF29	11	LXI D,FF34				
FF2A	34					
FF2B	FF					
FF2C	26	MVI H,00				

ADDRESS	DATA	DESCRIPTION
FF34	40	(PATTERN FOR "0")
FF35	79	(PATTERN FOR "1")
FF36	24	(PATTERN FOR "2")
FF37	30	(PATTERN FOR "3")
FF38	19	(PATTERN FOR "4")
FF39	12	(PATTERN FOR "5")
FF3A	02	(PATTERN FOR "6")
FF3B	78	(PATTERN FOR "7")
FF3C	00	(PATTERN FOR "8")
FF3D	18	(PATTERN FOR "9")
FF3E	08	(PATTERN FOR "A")
FF3F	03	(PATTERN FOR "B")
FF40	46	(PATTERN FOR "C")
FF41	21	(PATTERN FOR "D")
FF42	06	(PATTERN FOR "E")
FF43	0E	(PATTERN FOR "F")
FF44	D5	PUSH D
FF45	F5	PUSH PSW
FF46	CD	CALL FF58
FF47	58	
FF48	FF	
FF49	11	LXI D,00FF
FF4A	FF	
FF4B	00	
FF4C	1B	DCX D
FF4D	7A	MOV A,D
FF4E	B3	ORA E
FF4F	C2	JNZ FF4C
FF50	4C	
FF51	FF	
FF52	CD	CALL FF5D
FF53	5D	
FF54	FF	
FF55	F1	POP PSW
FF56	D1	POP D
FF57	C9	RET
FF58	1E	MVI E,00
FF59	00	
FF5A	C3	JMP FF5F
FF5B	5F	
FF5C	FF	
FF5D	1E	MVI E,FF
FF5E	FF	
FF5F	0E	MVI C,0E
FF60	0E	
FF61	CD	CALL 1000
FF62	00	
FF63	10	
FF64	C9	RET

Scanning the Keypad

To read a 4 by 4 matrix keypad we need 4 inputs and 4 outputs. The 4 inputs will check for a key pressed in one of the 4 columns in the current row selected by the 4 outputs. Since all of the outputs are currently being used, where do we get 4 more? We will use the same ones used for the displays but we will only use them while the displays are off (this is why we needed the circuitry to turn off both displays).

The subroutine KEYSN (shown below), which will be added to the previous program, will be CALLED while the digits are off so that the changes in the output port will not be visible. When a key is pressed, the routine will modify the B register by shifting it left 4 bits and putting the binary value of the key into the lower 4 bits.

When KEYSN is CALLED, output bits 0 to 3 are set to 0 to select all 4 rows

at once. When the input port is read and all of the lower 4 bits are 1, this indicates no key is pressed and the routine is exited without changing B. If any of the lower 4 bits are 0 this indicates a key has been pressed. The routine then selects 1 row at a time (by setting 1 of the output bits to 0 and the others to 1) until the input port reads a 0 on any of the lower 4 bits. When this happens, the row is found, and the column is found by finding which input port bit was 0. When the row and column is found it is translated to a value from 0 to F hex. The B register is shifted 4 bits to the left and this new value is put in the lower 4 bits and the routine exits.

There is another feature in KEYSCN which keeps a key that is being held closed from modifying the B register more than 1 time. When a key is pressed, the H register is loaded with a value which defines the minimum number of times KEYSCN must be CALLED while no key is pressed before it will recognize another key press. For example, when a key is pressed, B is modified by the new key value and H is loaded with 20 hex before exiting KEYSCN. On the next entry to KEYSCN the keypad will be examined to see if a key has been pressed and if one is pressed, H is not decremented and the routine is exited without changing B. If no keys are being pressed, H is decremented and the routine is exited without changing B. If no keys are pressed for 32 (20 hex) CALLS of KEYSCN then H will be 0 and any key pressed after this time will affect the B register, and again, H will be loaded with 20 hex.

```

;
; This routine checks for a key pressed and if there is one, register B
; is shifted left one nibble and the key value is put in the low nibble.
; The subsequent CALLs after a CALL that affected B, will not affect B
; again until no key has been pressed for 20 CALLs and then a key is
; pressed again. This prevents a single key press from being
; interpreted as more than one.
;
; On entry and exit: H=debounce counter
;
DBOUNCE EQU 20 ;NUMBER OF CALLs FOLLOWING A KEY PRESS
KEYSCN: XRA A ;A=0
        OUT OPORT ;SELECT ALL 4 ROWS
        IN IPORT ;READ ALL 4 ROWS OF KEYPAD
        ANI 0FH ;MASK OFF UPPER 4 BITS
        CPI 0FH ;IF 0FH THEN NO KEYS PRESSED
        JNZ KEYSC1 ;SKIP IF KEY READY

        ; NO KEY PRESSED, SO DEC. THE DEBOUNCE (IF>0) AND EXIT
        INR H
        DCR H ;IS DEBOUNCE 0?
        RZ ;RETURN IF YES
        DCR H ;DEC ONCE MORE
        RET

KEYSC1: INR H
        DCR H
        RNZ ;IF DEBOUNCE <> 0 EXIT

        ; SCAN FOR SPECIFIC ROW
        PUSH D
        MVI E,01111111B ;ROW SCAN VALUE (WILL BE ROTATED)
        MVI D,-4 ;ROW ADDER (+4=0)

KEYSC2: MOV A,E ;GET ROW SCAN VALUE
        RLC ;ROTATE IT
        OUT OPORT ;SEND ROW SCAN TO OUTPUT PORT
        MOV E,A ;SAVE BACK NEW ROW SCAN

        MOV A,D ;GET ROW ADDER
        ADI 4 ;INC ROW ADDER BY 4
        MOV D,A ;SAVE IT

```

```

IN      IPORT      ;SEE IF THIS ROW HAS CHAR READY
ANI     0FH        ;MASK OFF UPPER
CPI     0FH
JZ      KEYSC2     ;LOOP TILL <> 0FH

; FIND WHAT COL. IT'S IN
KEYPD1: MVI     L,0FFH      ;SET SO INR WILL MAKE 0
INR     L
RRC
JC      KEYPD1     ;LOOP TILL NO CY
; NOW ADD COL. TO ROW ADDER
MOV     A,D        ;GET ROW ADDER
ADD     L
MOV     L,A        ;L IS THE KEY PRESSED (0 TO F HEX)
; SHIFT B LEFT 1 NIBBLE AND PUT L IN LOWER NIBBLE
MOV     A,B        ;SHIFT B
ADD     A
ADD     A
ADD     A
ADD     A          ;THIS SHIFTS LEFT PADDING 0's
ADD     L          ;PUT L IN LOWER NIBBLE
MOV     B,A        ;NEW B REG

MVI     H,DBOUNCE  ;DEBOUNCE VAL. (NO KEYS ACCEPTED TILL 0)
POP     D
RET

```

Using the Program

The previous program will be modified slightly (assuming it is still in memory) by putting CALL KEYSCN in the program in place of IN IPORT, MOV B,A and a new subroutine will be added at the end. (Pay close attention to the addresses when entering the following program, since there is a skip in sequence of the addresses after the first three.) When you run the program you should see the key you press on the right display and the digit that was there before, moved to the left display. As you have just seen demonstrated in this application, multiplexing allows you to greatly extend the capabilities of an output port.

ADDRESS	DATA	DESCRIPTION	FF7B	7F		
FF01	CD	CALL FF65	FF7C	16	MVI	D,FC
FF02	65		FF7D	FC		
FF03	FF		FF7E	7B	MOV	A,E
:	:		FF7F	07	RLC	
:	:		FF80	D3	OUT	11
FF65	AF	XRA A	FF81	11		
FF66	D3	OUT 11	FF82	5F	MOV	E,A
			FF83	7A	MOV	A,D
FF67	11					
FF68	DB	IN 12	ADDRESS	DATA	DESCRIPTION	
FF69	12		FF84	C6	ADI	04
FF6A	E6	ANI 0F	FF85	04		
FF6B	0F		FF86	57	MOV	D,A
FF6C	FE	CPI 0F	FF87	DB	IN	12
FF6D	0F		FF88	12		
FF6E	C2	JNZ FF76	FF89	E6	ANI	0F
FF6F	76		FF8A	0F		
FF70	FF		FF8B	FE	CPI	0F
FF71	24	INR H	FF8C	0F		
FF72	25	DCR H	FF8D	CA	JZ	FF7E
FF73	C8	RZ	FF8E	7E		
FF74	25	DCR H	FF8F	FF		
FF75	C9	RET	FF90	2E	MVI	L,FF
FF76	24	INR H	FF91	FF		
FF77	25	DCR H	FF92	2C	INR	L
FF78	C0	RNZ	FF93	0F	RRC	
FF79	D5	PUSH D	FF94	DA	JC	FF92
FF7A	1E	MVI E,7F	FF95	92		

FF96	FF		
FF97	7A	MOV	A, D
FF98	85	ADD	L
FF99	6F	MOV	L, A
FF9A	78	MOV	A, B
FF9B	87	ADD	A
FF9C	87	ADD	A
FF9D	87	ADD	A
FF9E	87	ADD	A
FF9F	85	ADD	L
FFA0	47	MOV	B, A
FFA1	26	MVI	H, 14
FFA2	14		
FFA3	D1	POP	D
FFA4	C9	RET	